

LM5068 -48V Hot Swap Controller

National Semiconductor
Application Note 1304
Ravi Murugesappa
January 2004



Introduction

LM5068 is a hot-swap controller that allows a circuit card to be safely inserted or removed from live backplane without having to shutdown the system power. The wide operating input voltage range (from -10V to -90V) is well suited for -48V power systems. The LM5068 provides a current limited power to turn-on circuit cards thus preventing glitches on the power supply rail and damage to board connectors and components. The under-voltage and over-voltage protection of the LM5068 ensure that the input voltage is stable and within tolerance before applying power to the load.

This application note explains the function and design of components connected to MOSFET's gate terminal which limit inrush currents during insertion of a module into a live backplane when using the LM5068 without external current sense resistor.

Theory of Operation

LM5068 is a hot-swap controller used as system supply monitor as well as current limiter. The system monitor function senses the supply voltage for under-voltage and over-voltage conditions and will shutdown the external MOSFET to stop power from flowing to load during these conditions. The current monitor functions to limit inrush current and output overload circuit current to prevent damage to the system.

LM5068 has three current limit thresholds, at 50mV , 100mV and 200mV , to limit overload circuit current during output short-circuit or other overload conditions using current sense

resistor. From the above current limit thresholds, it is clear that overload current limit threshold of 100mV (IACL, active current limit loop) is twice the circuit breaker (ICB) current limit of 50mV , and the user doesn't always have the flexibility to set his inrush current limit to twice the steady state current limit threshold of 50mV , due to application limitations. This application note describes an alternative approach to overcome these situations without the use of current-sense resistor.

In the application circuit shown below *Figure 1*, the input power to the module (shown here as load) is controlled by placing an N-channel external MOSFET switch in the power path. Resistors R1,R2 & R3 determine the UV and OV thresholds of the power supply input. Both the controller (LM5068) and the external MOSFET work together to limit the charging current when the board is first plugged into the live backplane. When the power is first applied to VDD, the controller holds the gate of the MOSFET (Q1) to ground. After a programmable debounce delay determined by the timer capacitor CT, an internal $60\mu\text{A}$ current source begins to charge the MOSFET gate. The capacitor C2 and resistor R4 acts as a feedback network to accurately control the dv/dt and inrush current in the load capacitor CL. The drain voltage fall rate as the MOSFET turns on, is fed back to the gate terminal through R4 and C2, to appropriately control the gate voltage rise time. The MOSFET gate is supplied by a constant current source of $60\mu\text{A}$. The desired value of capacitor C2 can be calculated as follows. Refer to the schematic below *Figure 2*.

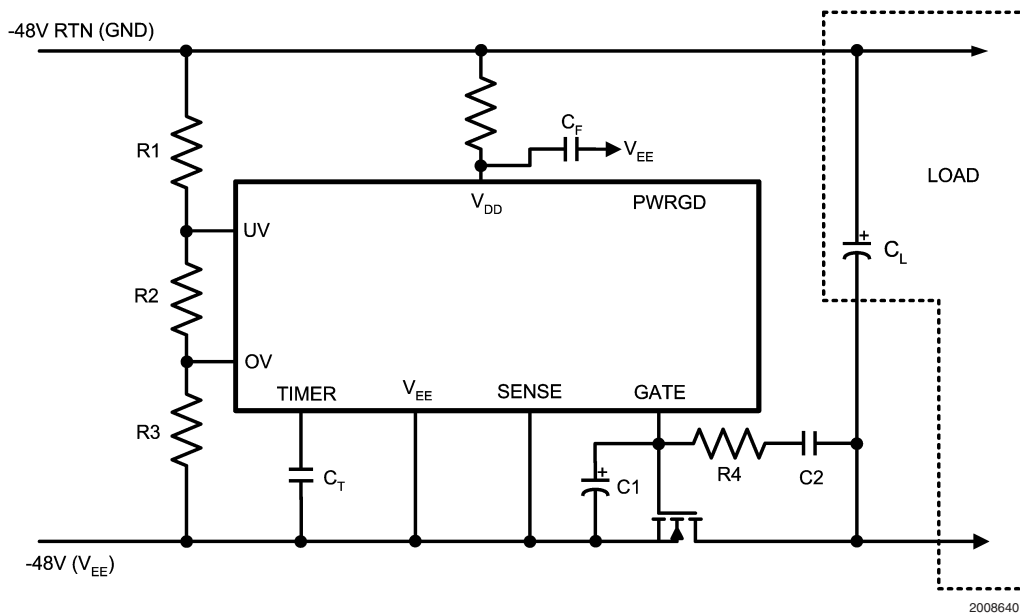


FIGURE 1. Typical Application Schematic

Theory of Operation (Continued)

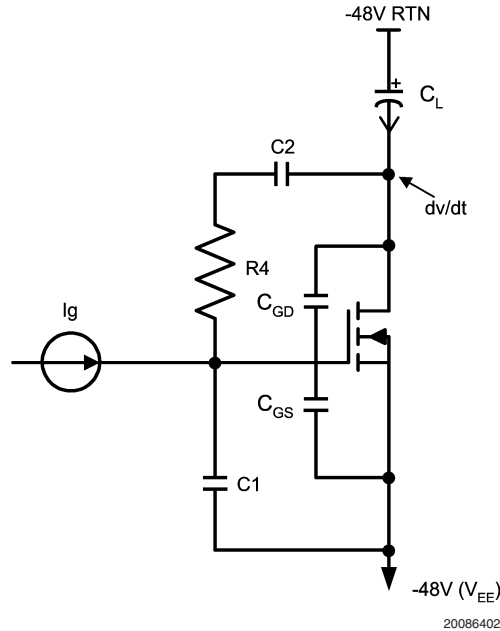


FIGURE 2. Calculation of Feedback Capacitor C2

The rate of change of drain voltage is given by,

$$\frac{dv}{dt} = \frac{I_g}{(C_2 + C_{GD})} = \frac{I_{L(max)}}{C_L} \quad (1)$$

where I_g is the gate current source, and $I_{L(max)}$ is the maximum inrush current that is allowed, and C_{GD} is the MOSFET's gate to drain capacitance.

From equation (1), C_2 can be calculated as

$$C_2 + C_{GD} = C_L \times \frac{I_g}{I_{L(max)}} \quad (2)$$

$$C_2 = C_L \times \frac{I_g}{I_{L(max)}} - C_{GD} \quad (3)$$

R_4 is calculated to limit current and to have a maximum drop of less than a volt at $60\mu A$ of MOSFET gate current, and to eliminate any kind of glitch at the gate terminal during normal operation or during plugging into the live backplane using R_4 , C_1 filter. Capacitor C_1 and R_4 prevent Q1 from turning on momentarily when the power pins first make contact. Without C_1 and R_4 , Capacitor C_2 would pull up the gate of

Q1 to approximately even before the LM5068 powers up and the pull-down of the gate is activated.

$$V_g = |V_{EE}| \times \frac{C_2 + C_{GD}}{C_{GS}} \quad (4)$$

In the above equation, C_{GS} is the internal gate to source capacitance of the MOSFET. By placing capacitor C_1 in parallel with gate to source capacitance of Q1, this issue can be avoided. The value of C_1 is calculated as follows.

$$C_1 \geq \left[\frac{(V_{IN(max)} - V_{th})}{V_{th}} \times (C_2 + C_{GD}) \right] - C_{GS} \quad (5)$$

where V_{th} is MOSFET's minimum gate threshold voltage and C_{GD} is the gate to drain capacitance of the MOSFET.

Conclusion

This application note describes the functionality of LM5068 hot-swap controller as a inrush current limiter and system monitor without using a current sense resistor. It should be understood that without sense resistor some features of LM5068 are disabled, including limiting output overload circuit current and excessive supply currents.

Notes

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor certifies that the products and packing materials meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.



National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959

www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560