



1.0 Design Specifications

Inputs	Outputs #1	Outputs #2
VinMin=36	Vout1=3.3	Vout2=1.8
VinMax=57	Iout1=2	Iout2=1

2.0 Design Description

The LM2698 is used to design a fully isolated forward converter power supply. The output inductor, L1, is augmented by a secondary winding to make a coupled-inductor (transformer) for creating a second low cost linear output. The linear output uses the LP2986 augmented with an additional pass transistor, Q2, to drive up to 1A of current. The LM2698 is a PWM regulator with internal low-side FET switch. The cascode FET stage, M1, provides a low cost means to protect the regulator IC from the high input voltage while providing very fast switching.

A forward converter architecture is mathematically analogous to a step-down, buck architecture with its Duty Cycle multiplied by the turns-ratio of the transformer, T1. The input

voltage is effectively chopped by the switching action of the regulator's internal switch so that the AC signal can be passed through and reduced by the transformer. The AC voltage pulses at the voltage switch node connecting diode D5, fly-back diode D4, and the LC filter, L1 & C6 & C12, act to create the correct output voltage as a function of the regulator switch duty cycle.

The LM3411 is a shunt regulator acting as feedback error amplifier plus reference while the opto-coupler provides dc isolation (between the primary and secondary sides supply) for the feedback path of the loop.

Notes: M1 in the schematic is displayed as Q2 in the layout. Q2 in the schematic is Q3 in the layout.

3.0 Schematic


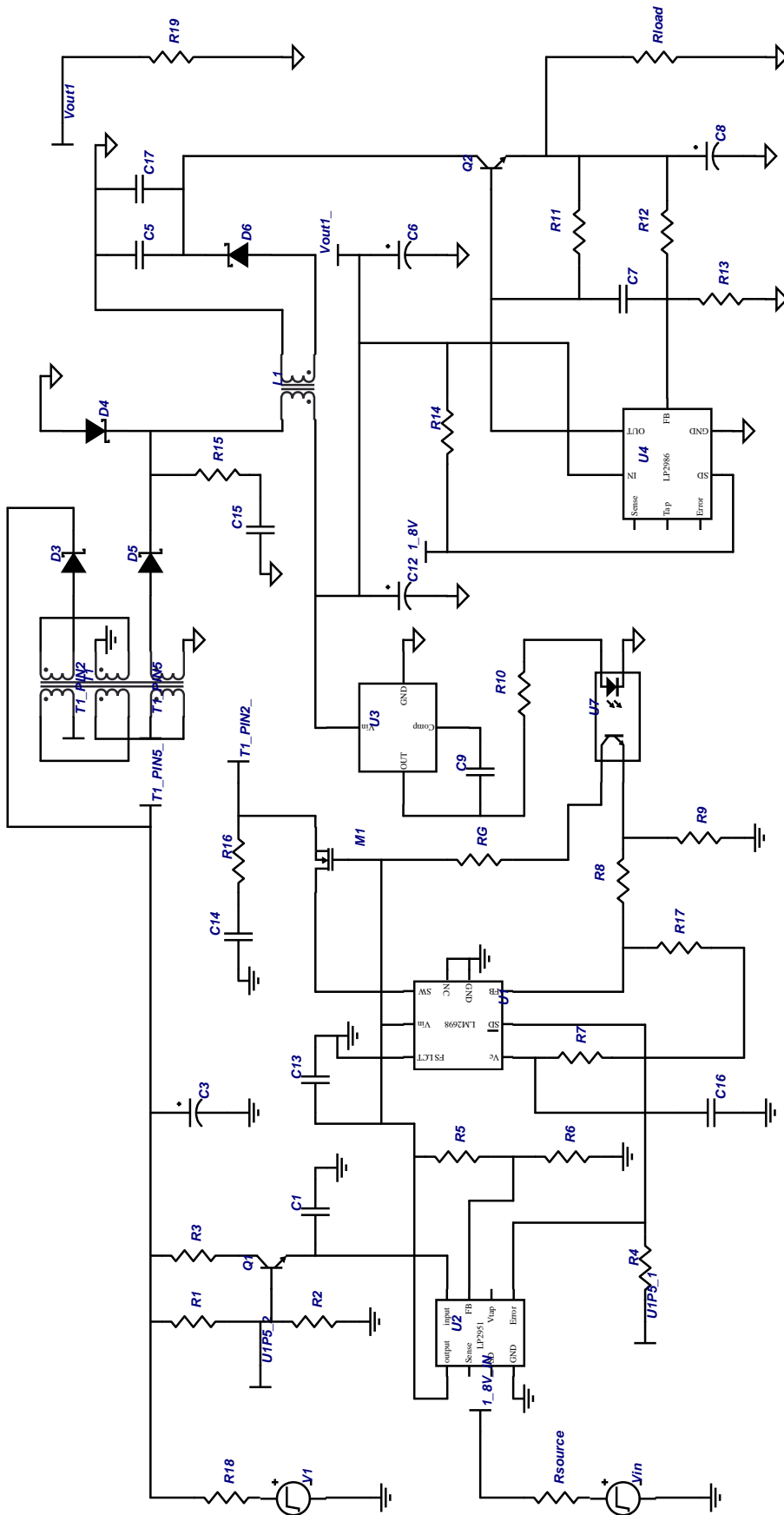


FIGURE 1. Example Schematic Showing Connection for all Components.

4.0 Bill Of Materials


Part	Manufacturer	Part#	Attributes
C1	TDK	C2316X7R1E105K	1u F
C12	TDK	C3216X5R0J106M	10u F
C13	TDK	C3216X7R1E105K	1u F
C14	NOT USED	NOT USED	0 F
C15	Vishay	VJ1206A102KXAAT	1000p F
C16	Vishay	VJ1206A101KXAAT	100p F
C17	Vishay	594D107X9016D2T	100u F
C5	TDK	C3216X5R0J106M	10u F
C6	Vishay	594D337X96R3D2T	330u F
C7	Vishay	VJ1206A102KXAAT	1n F
C8	Vishay	594D107X9016D2T	100u F, 0.06 Ohms
C9	Vishay	VJ1206Y123KXXAT	12n F
D3	ONSEMI	MURS120	0.875 V
D4	ONSEMI	MBRS240	0.43 V
D5	ONSEMI	MBRS240	0.43 V
D6	ONSEMI	MBRS240	0.43 V
L1	Pulse	PO398	23.1u H, 0.0597 Ohms
M1	Fairchild	MMBTA42	
Q1	ONSEMI	FDS2670	
Q2	ONSEMI	MMJT9410	
R1	Vishay	CRCW12062002FRT6	20k Ohms
R10	Vishay	CRCW12061001FRT6	1k Ohms
R11	Vishay	CRCW12061000FRT6	100 Ohms
R12	Vishay	CRCW12064700FRT6	470 Ohms
R13	Vishay	CRCW12061001FRT6	1k Ohms
R14	Vishay	CRCW12061002FRT6	10k Ohms
R15	Vishay	CRCW12062R7JRT6	2.7 Ohms
R16	NOT USED	NOT USED	
R17	Vishay	CRCW12061003FRT6	100k Ohms
R2	Vishay	CRCW12061002FRT6	10k Ohms
R3	Vishay	CRCW12062001FRT6	2k Ohms
R4	Vishay	CRCW12061003FRT6	100k Ohms
R5	Vishay	CRCW12067502FRT6	75k Ohms
R6	Vishay	CRCW12061212FRT6	12.1k Ohms
R7	Vishay	CRCW12062003FRT6	200k Ohms
R8	Vishay	CRCW12063003FRT6	300k Ohms
R9	Vishay	CRCW12062001FRT6	2k Ohms
RG	Vishay	CRCW12063921FRT6	3.92k Ohms
T1	Coiltronics	VP2-1600	
U1	National Semiconductor	LM2698	
U2	National Semiconductor	LP2951	
U3	National Semiconductor	LM3411	
U4	National Semiconductor	LP2986	
U7	Vishay-Semiconductor	CNY-17F3	

5.0 Layout

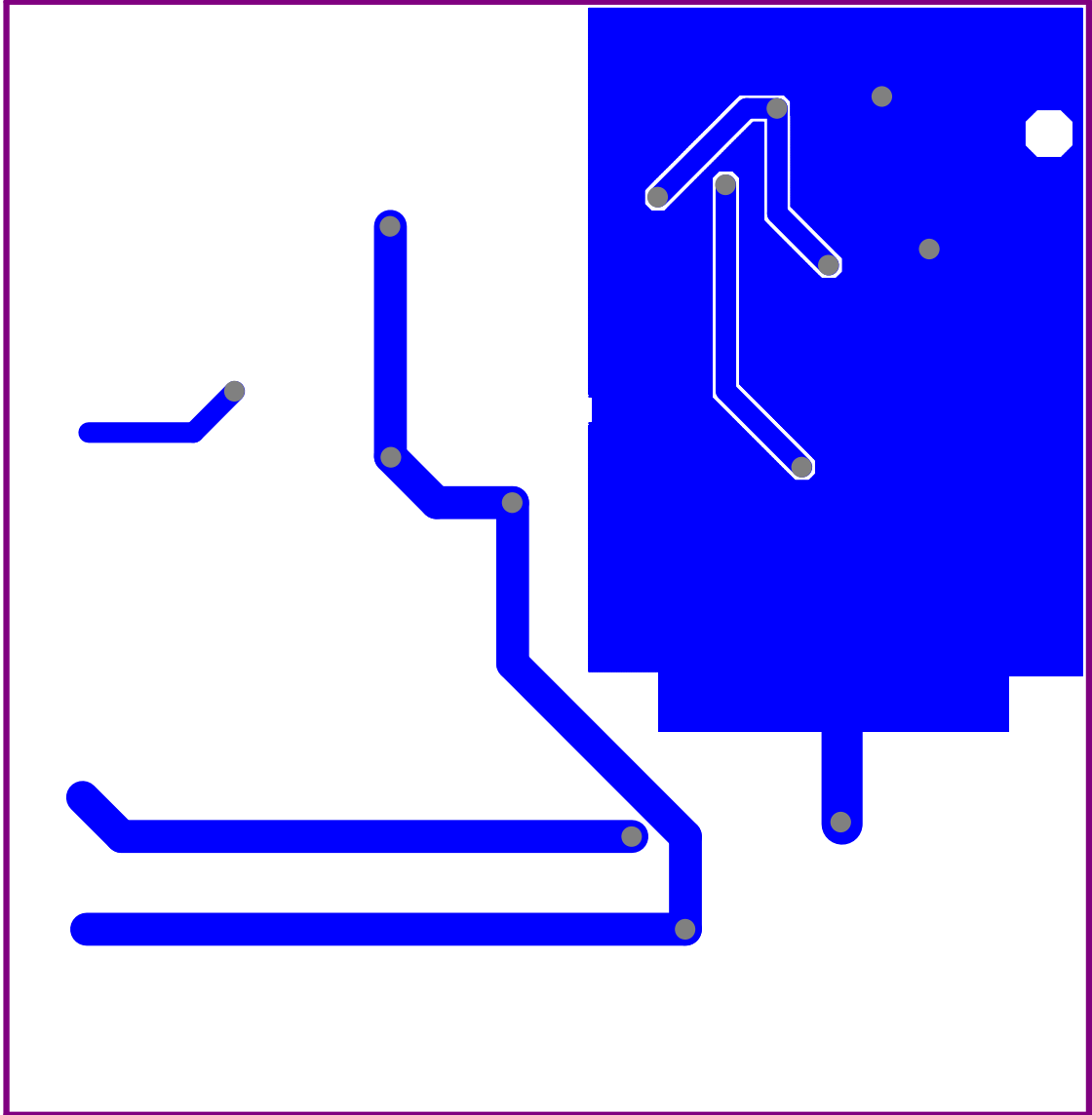

PADC_NSC0086_lo_1

FIGURE 2. Board's Bottom View

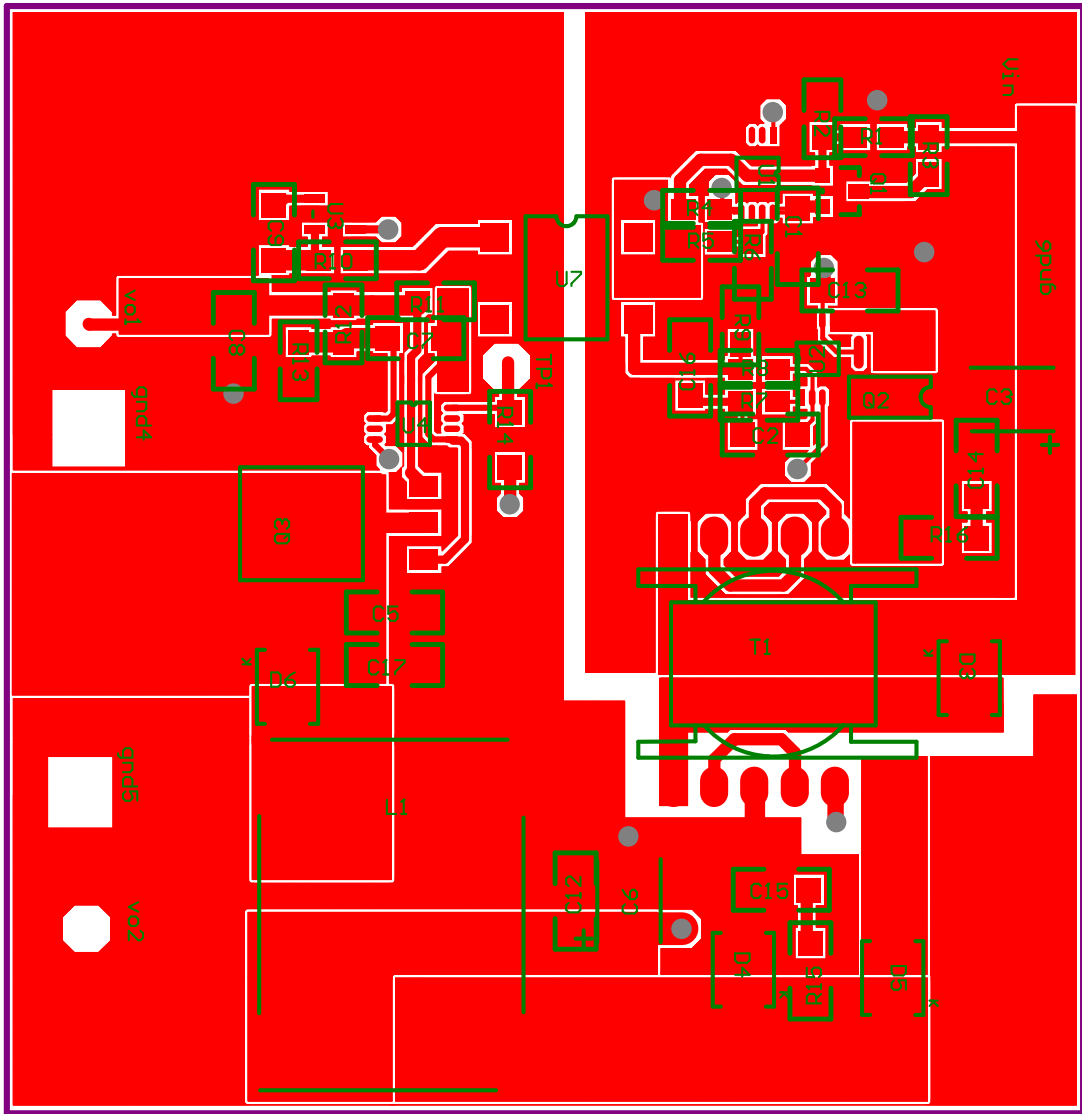

PADC_NSC0086_lo_2

FIGURE 3. Board's Top View

Notes

National Semiconductor's design tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Reference designs are created using National's published specifications as well as the published specifications of other device manufacturers. While National does update this information periodically, this information may not be current at the time the reference design is built. National and/or its licensors do not warrant the accuracy or completeness of the specifications or any information contained therein. National and/or its licensors do not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. National and/or its licensors do not warrant that the designs are production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which,
 - (a) are intended for surgical implant into the body, or
 - (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor certifies that the products and packing materials meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



National Semiconductor Americas Customer Support Center
 Email: new.feedback@nsc.com
 Tel: 1-800-272-9959

National Semiconductor Europe Customer Support Center
 Fax: +49 (0) 180-530-85-86
 Email: europe.support@nsc.com
 Deutsch Tel: +49 (0) 69 9508 6208
 English Tel: +49 (0) 870 24 0 2171
 Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Support Center
 Email: ap.support@nsc.com

National Semiconductor Japan Customer Support Center
 Fax: 81-3-5639-7507
 Email: jpn.feedback@nsc.com
 Tel: 81-3-5639-7560