



1.0 Design Specifications

Inputs	Outputs #1
VinMin=-57	Vout1=5.0
VinMax=-36	Iout1=1.4

2.0 Design Description

This design utilizes the LM5070 configured in a non-synchronous, flyback topology and operating in continuous conduction mode (CCM), to offer a low-cost, high efficiency solution for Power-over-Ethernet (PoE) applications*. The LM5070 is a dedicated PoE powered device (PD) interface/PWM controller that integrates all the power sequencing, control mode, and fault protection necessary to comply with the IEEE 802.3af specification for power sourcing equipment (PSE).

This non-isolated PoE design operates at 260kHz and uses a custom PoE transformer to convert the input voltage, via

flyback action, to an output voltage level of 5V at 1.4A (7W). The primary side bias is derived from an auxiliary winding after successful start-up occurs. The secondary side feedback components are selected appropriately to ensure proper gain and phase margins for stable operation and quick transient response.

* Refer to POWER Designer, No. 104 (<http://www.national.com/an/AN/AN-1358.pdf>) or the LM5070 Evaluation Board - Application Note 1358 (http://www.national.com/appinfo/power/files/PowerDesigner_104.pdf) for more information on Power Supply Design for PoE Applications.

3.0 Schematic

FIGURE 1. Example Schematic Showing Connection for all Components.

4.0 Bill Of Materials

Part	Manufacturer	Part#	Attributes
C1	TDK	C4532X7R2A225	2.2u F
C10	Vitramon	VJ0805A102KXXAT	1n F
C14	TDK	C3216X5R0J106K	10u F
C15	TDK	C3216X5R0J106K	10u F
C16	Sanyo	6CV390EX	390u F
C18	Vitramon	VJ0805A101KXXAT	100p F
C19	Vitramon	VJ0805A222KXAAT	2.2n F
C2	TDK	C4532X7R2A225	2.2u F
C3	TDK	C4532X7R2A225	2.2u F
C4	Vitramon	VJ0805A104KXAAT	0.1u F
C5	Vitramon	VJ0805A224KXAAT	0.22u F
C6	Vitramon	VJ0805A104KXAAT	0.1u F
C7	Vitramon	VJ0805A473KXAAT	47n F
C9	TDK	C2012X5R1A105K	1u F
D1	Diodes	HD01	1 V
D2	Diodes	HD01	1 V
D3	Fairchild	MMSD4148	1 V
D5	IR	12CWQ03	0.47 V
DZ1	Diodes	SMAJ60A	
J1	SAMTEC	MODS-A-8P8C-X	
L1	Coilcraft	DO1813P-181HC	0.18u H, 0.003 Ohms
M1	Vishay	SI4848DY	
R1	Dale	CRCW08051001FRT6	1k Ohms
R10	Dale	CRCW08051073FRT6	107k Ohms
R13	Dale	CRCW080520R0FRT6	20 Ohms
R14	Dale	CRCW08051212FRT6	12.1k Ohms
R17	Dale	CRCW08052212FRT6	22.1k Ohms
R18	Dale	CRCW08057321FRT6	7.32k Ohms
R19	Dale	CRCW08051003FRT6	100k Ohms
R2	Dale	CRCW08055903FRT6	590k Ohms
R3	Dale	CRCW08053322FRT6	33.2k Ohms
R5	Dale	CRCW08052492FRT6	24.9k Ohms
R6	OPEN	OPEN	
R7	Dale	CRCW08051000FRT6	100 Ohms
R8	Dale	CRCW12060R60FRT6	0.6 Ohms
T1	Coilcraft	C1588-A	
U1	National Semiconductor	LM5070	

5.0 Layout

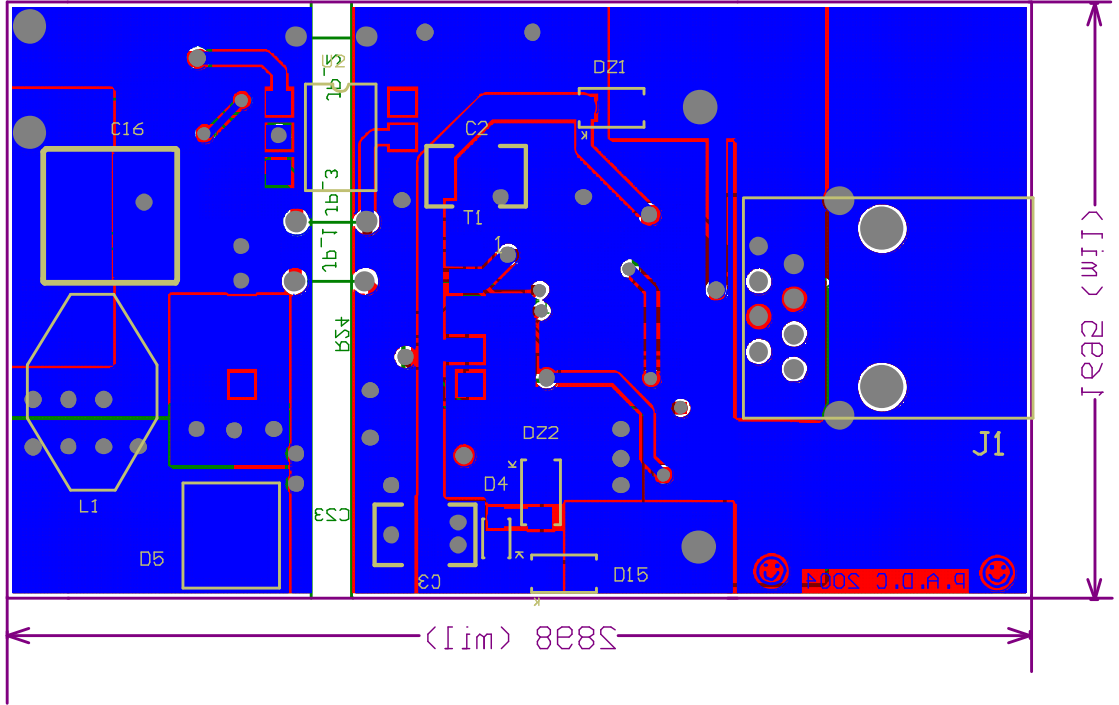


FIGURE 2. Board's Bottom View

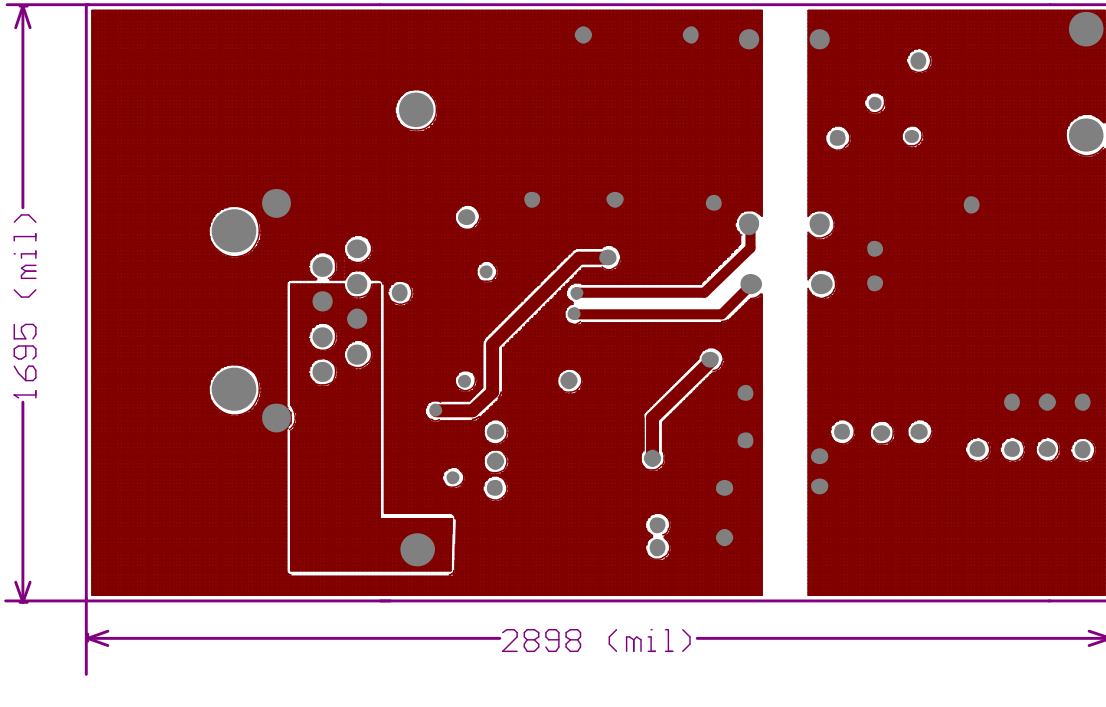


FIGURE 3. LM5070_PoE_pcb_mid1

PADC_POE_5V_7W_lo_2

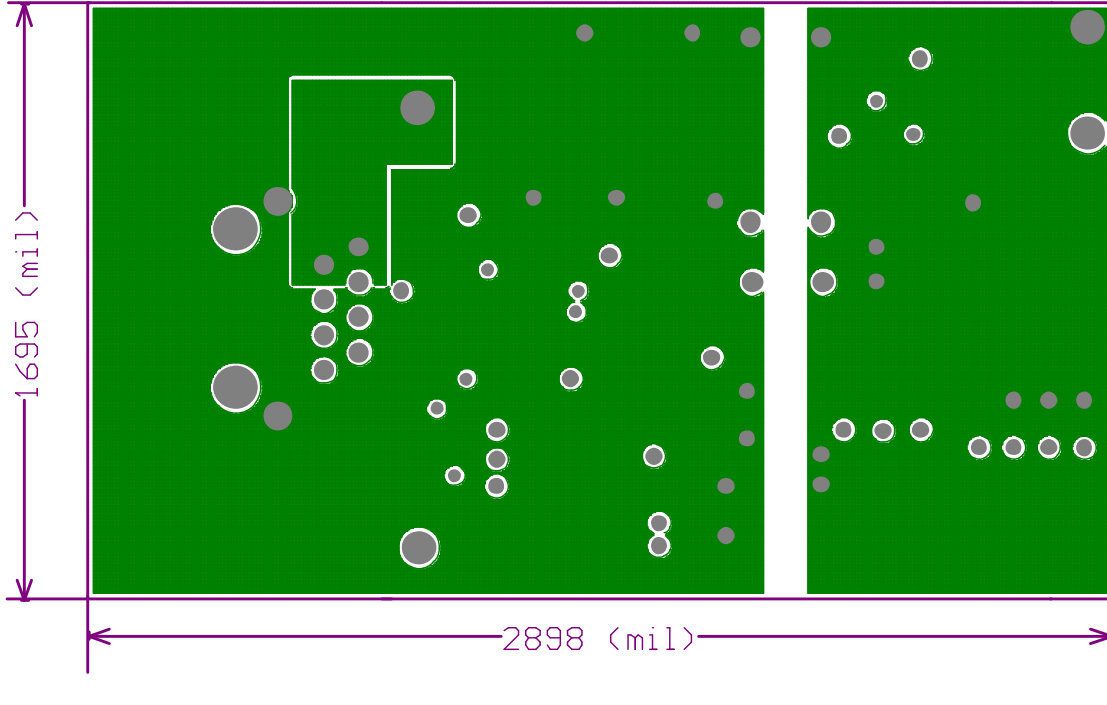


FIGURE 4. LM5070_PoE_pcb_mid2


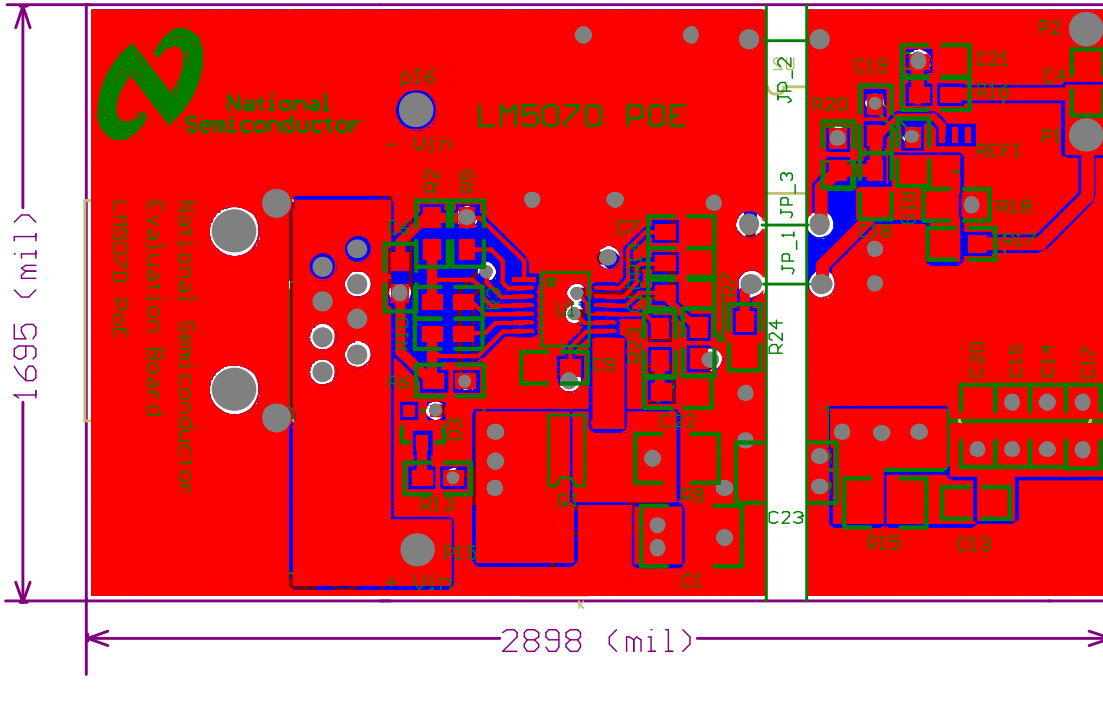


FIGURE 5. Board's Top View


PADC_POE_5V_7W_lo_4

6.0 Waveforms

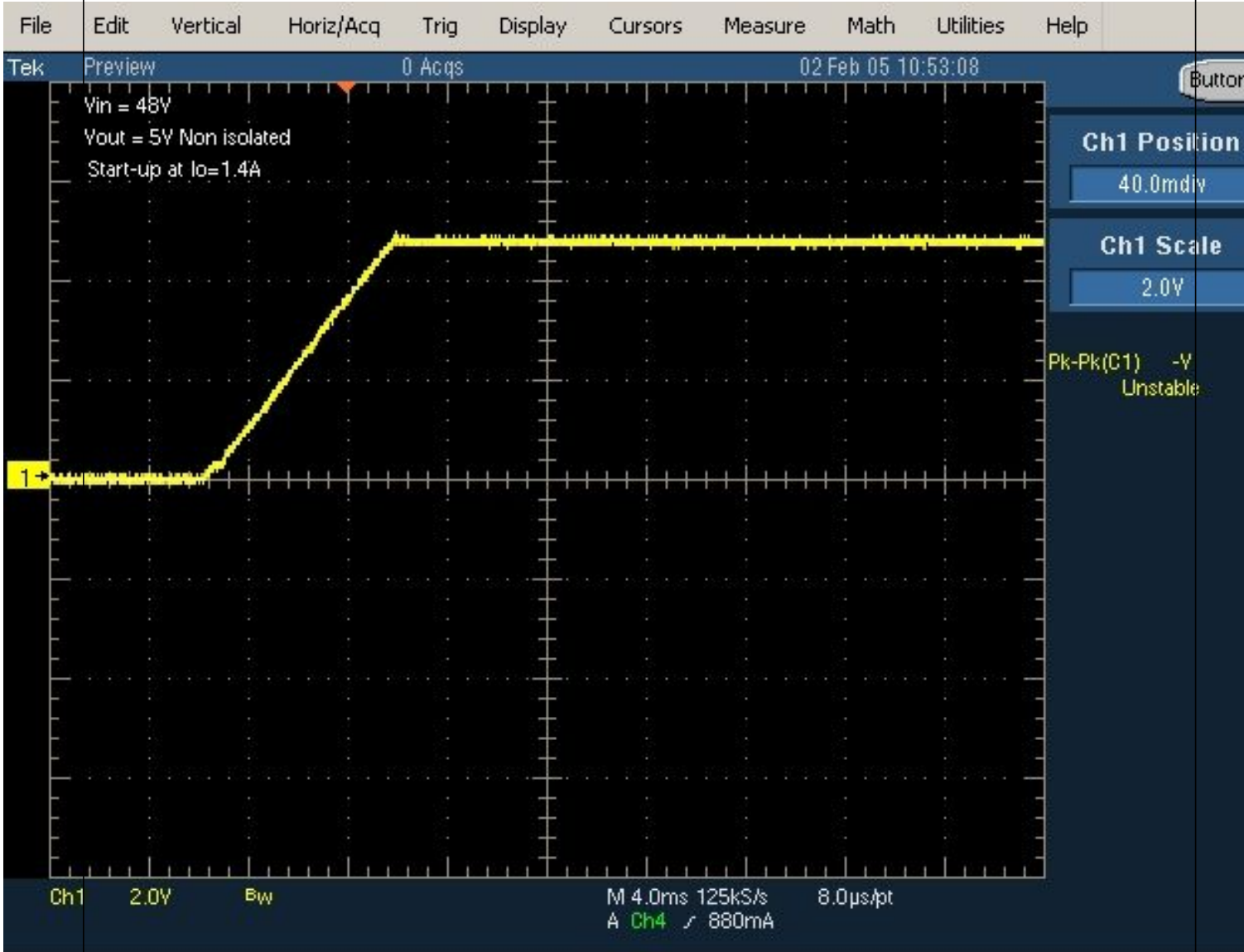


PADC_POE_5V_7V

FIGURE 6. Full load start-up

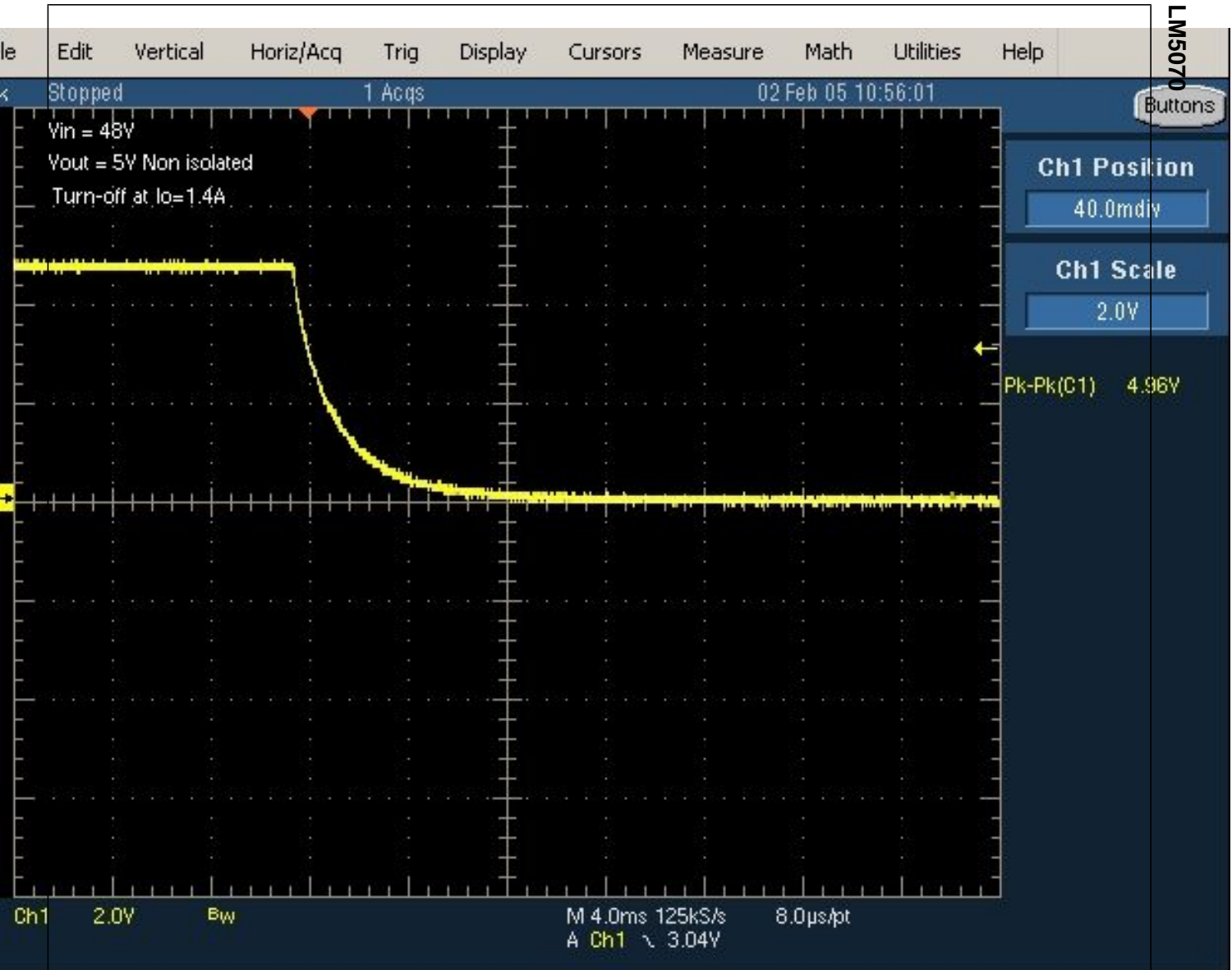

PADC_POE_5V_7W_wf_6

FIGURE 7. Full load turn-off

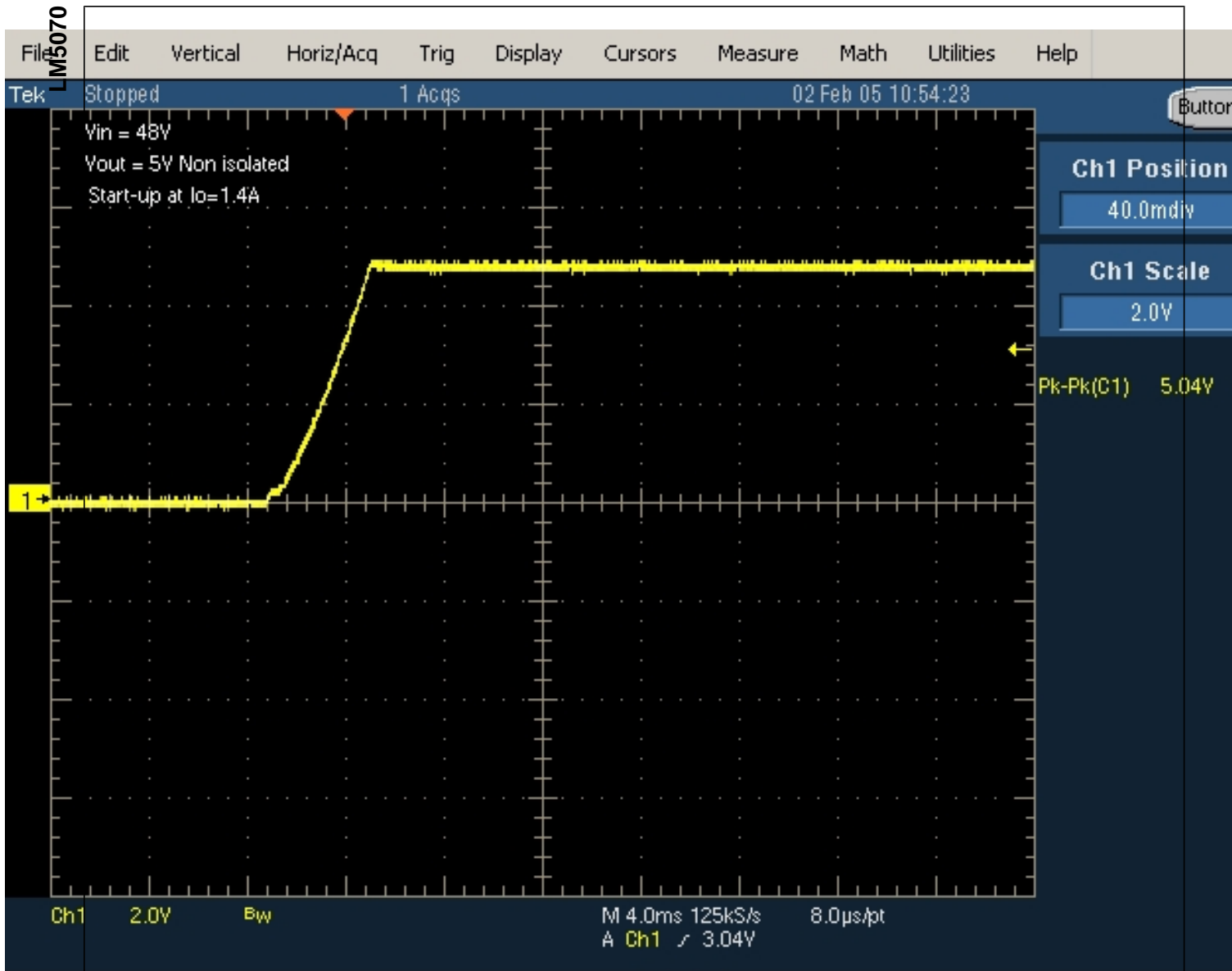

PADC_POE_5V_7W

FIGURE 8. No load start-up



PADC_POE_5V_7W_wf_8

FIGURE 9. Transient response


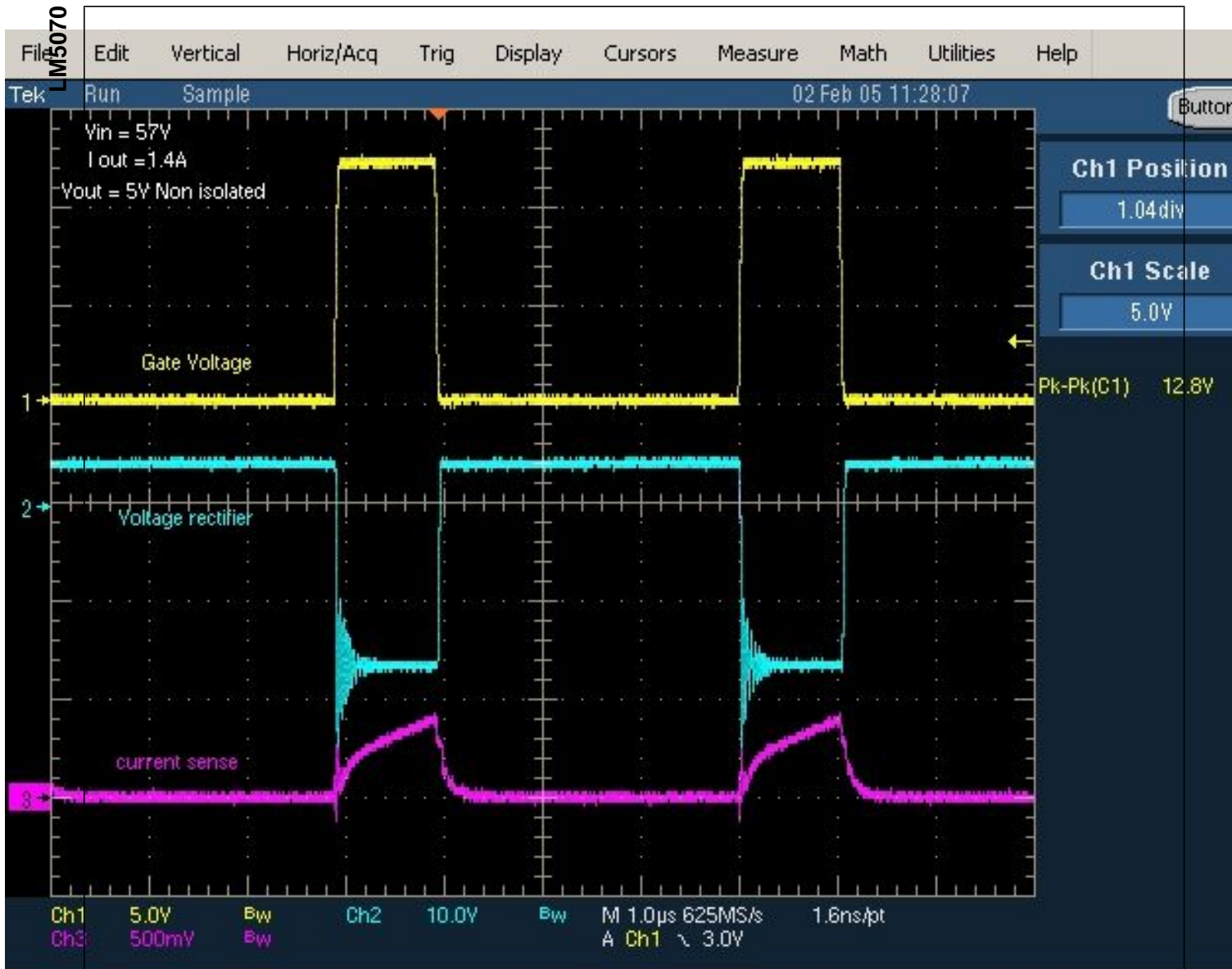


FIGURE 10. Vin=57V waveforms

PADC_POE_5V_7V

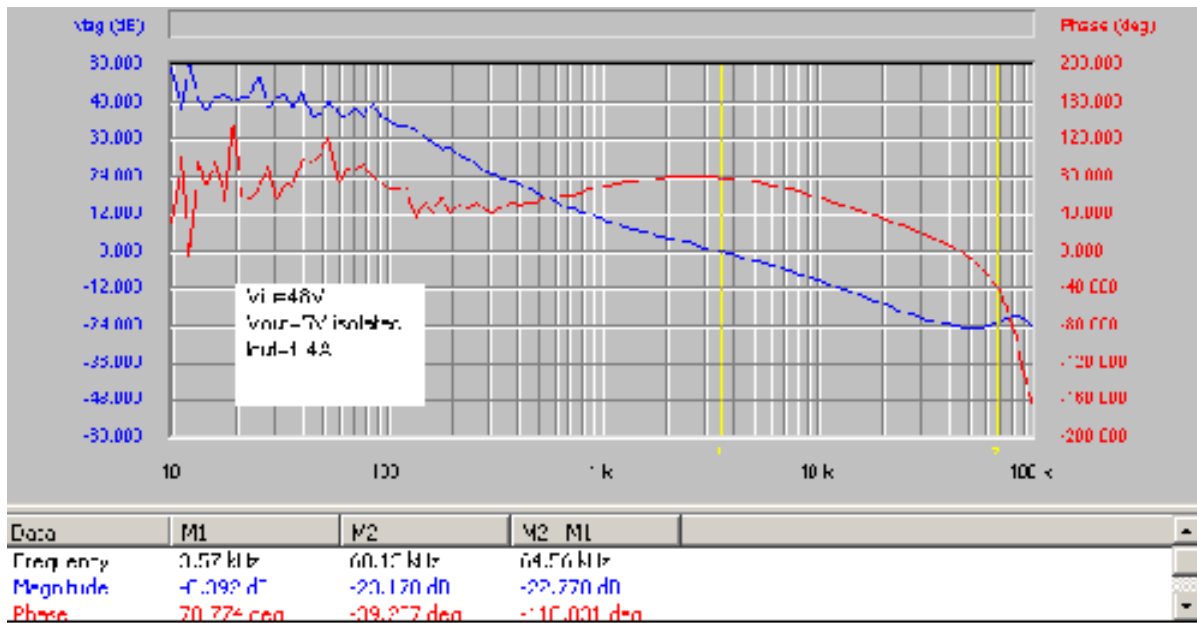

PAD0_POE_5V_7W_wf_10

FIGURE 11. Bode plots

Notes

National Semiconductor's design tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Reference designs are created using National's published specifications as well as the published specifications of other device manufacturers. While National does update this information periodically, this information may not be current at the time the reference design is built. National and/or its licensors do not warrant the accuracy or completeness of the specifications or any information contained therein. National and/or its licensors do not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. National and/or its licensors do not warrant that the designs are production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which,
 - (a) are intended for surgical implant into the body, or
 - (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor certifies that the products and packing materials meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



National Semiconductor Americas Customer Support Center
 Email: new.feedback@nsc.com
 Tel: 1-800-272-9959

National Semiconductor Europe Customer Support Center
 Fax: +49 (0) 180-530-85-86
 Email: europe.support@nsc.com
 Deutsch Tel: +49 (0) 69 9508 6208
 English Tel: +49 (0) 870 24 0 2171
 Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Support Center
 Email: ap.support@nsc.com

National Semiconductor Japan Customer Support Center
 Fax: 81-3-5639-7507
 Email: jpn.feedback@nsc.com
 Tel: 81-3-5639-7560