

February 2008

## Emulated Ripple Mode – The Future of Hysteretic Switch Mode Power Supplies


By **Frederik Dostal**, National Semiconductor

### Introduction

Hysteretic control in switch mode power supplies has been around for a very long time. It is a very simple control mechanism which requires little control circuitry and does not need to get compensated for stability like voltage mode control and current mode control regulators. Instead of an error amplifier, the hysteretic control uses a hysteretic comparator to check if the output voltage is out of regulation. Hysteretic mode control is very fast when it comes to transient response and is easy to implement with a low build cost, But there are some disadvantages that come with it, such as a changing switching frequency and input voltage changes as well. It is also required to provide the hysteretic comparator with enough ripple for proper operation. This minimum ripple requirement usually leads to a certain output voltage ripple which may not be acceptable in some applications. Advances in hysteretic mode control were made to eliminate these disadvantages. Constant On Time (COT) was introduced to avoid the wide change of switching frequency upon line variations and Emulated Ripple Mode (ERM) is the newest achievement to avoid the need for output voltage ripple.

### How Does Hysteretic Mode Control Work?

Figure 1 shows the control schematic of hysteretic mode control. It is a very simple way to regulate a fixed output voltage. The necessary building blocks are a reference, a hysteretic comparator and a power stage which creates a pulse width modulation (PWM) duty-cycle based on the hysteretic comparator information.

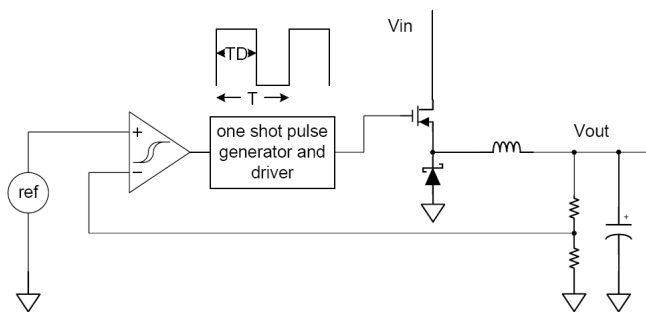


**Figure 1. Pure Hysteretic Mode Control**

When the output voltage is below the hysteretic comparators low threshold, an on time is initiated by the power stage. This on time is complete when the high threshold level of the hysteretic comparator is reached. By this the frequency is not constant, but dependent on how the output voltage changes during the on time as well as during the off time.

Hysteretic control does not require an internal oscillator. Switching frequency depends on the external components and operating conditions such as load current and line voltage since these parameters influence when the output voltage crosses the hysteretic comparator thresholds. The positive aspects of pure hysteretic mode control is the simple control concepts which requires little control circuitry. This makes hysteretic mode control solutions usually very low cost. Also hysteretic control is very fast and quickly adjusts for line and load transients. The disadvantage of such a control scheme is the varying switching frequency with the selection of power stage components, such as the inductor and output capacitor as well as the changing input voltage.

A second disadvantage is the requirement of ripple voltage at the input of the error comparator which is the feedback pin. If the ripple generated by the inductor current ripple and the output capacitor is phase shifted, the output voltage will not cross the hysteretic comparator thresholds in phase and the control scheme will not work smoothly. The result is burst mode operation and no continuous or clean switch node waveform.

When ceramic capacitors, which have very low ESR (equivalent series resistor), are used as output capacitors, the main voltage ripple generated is caused by the capacitance and not by the ESR of the component. This causes a sine wave like voltage ripple shifted by 90 degrees compared to a triangle like voltage ripple which is caused by an output capacitor with higher ESR. Figure 2 shows the waveforms of output voltage ripple with a ceramic capacitor and with an electrolytic capacitor.

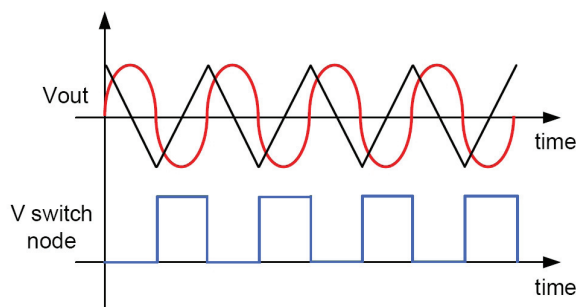

**Figure 2. Output voltage ripple caused by a ceramic capacitor and a higher ESR capacitor**

The black waveform is valid for capacitor types with higher ESR such as electrolytic capacitors. Here the output voltage ripple is in sync with the switch waveform. The red waveform shows the output ripple voltage with capacitors with very low ESR where the voltage ripple is not caused by the ESR but by the output capacitance itself. An example for a purely hysteretic mode controller is National Semiconductors LM3485.

